

ALTERNATING CURRENT (AC) – Class 12 Physics

Prepared in simple language, with colorful analogies, diagrams, formulas, solved numericals, PYQs, revision notes, exam hacks, and more.

1. THEORY IN SIMPLE WORDS (WITH VISUALS)


1.1 What is Alternating Current?

AC (Alternating Current) = current that keeps changing direction and magnitude with time.

Visual Analogy

Imagine water in a pipe moving forward then backward rhythmically.

Graph:

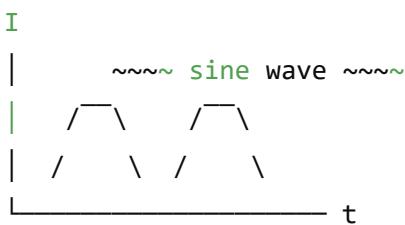

1.2 AC Voltage & Current

$$i = i_0 \sin(\omega t)$$

$$v = v_0 \sin(\omega t)$$

Where:

- i_0, v_0 = peak values
- ω = angular frequency
- T = time period
- f = frequency

$$\omega = 2\pi f = \frac{2\pi}{T}$$

1.3 RMS (Root Mean Square)

AC does not have constant value → we use "effective value".

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

Memory Trick:
"Divide peak by 1.414"

1.4 AC Circuit Elements


Resistor (R)

No phase difference:

V in phase with I

Inductor (L)

Current **lags** voltage by 90°.

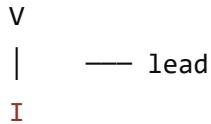

Capacitor (C)

Current **leads** voltage by 90°.

Mnemonic:

"ICE" → In Capacitor, Current leads

"LIV" → In Inductor, Voltage leads

1.5 Reactance

Inductive Reactance

$$X_L = \omega L = 2\pi f L$$

Capacitive Reactance

$$X_C = \frac{1}{\omega C}$$

1.6 Impedance of LCR Series Circuit

R + L + C in series

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Phase angle:

$$\tan \phi = \frac{X_L - X_C}{R}$$

🌈 1.7 Resonance in LCR Circuit

At resonance:

$$X_L = X_C$$

$$Z = R \text{ (minimum)}$$

$$I = I_{max}$$

Resonant frequency:

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Visual:

Resonance = maximum glow of bulb in LCR circuit

🌈 1.8 Power in AC Circuit

$$P = VI \cos \phi$$

$\cos \phi$ = power factor

Special cases:

- Pure R $\rightarrow \cos \phi = 1$ (maximum power)
 - Pure L or C $\rightarrow \cos \phi = 0$ (no power consumed)
-

⭐ 2. KEY CONCEPTS & FORMULAS TABLE

Quantity	Formula	Notes
AC current	$i = i_0 \sin \omega t$	sinusoidal
RMS value	$I_0/\sqrt{2}$	effective
Inductive reactance	$X_L = \omega L$	increases with f
Capacitive reactance	$X_C = 1/\omega C$	decreases with f
Impedance	$Z = \sqrt{R^2 + (X_L - X_C)^2}$	AC resistance
Power	$P = VI \cos \phi$	power factor
Resonance	$f_r = 1/(2\pi\sqrt{LC})$	max current

Mnemonics

The famous one: ELI-ICE

- E L I → Voltage (E) leads current (I) in L
- I C E → Current (I) leads voltage (E) in C

Power Factor

"Cosφ tells the truth"

(Real power = $VI\cos\phi$)

3. SOLVED NUMERICAL PROBLEMS

Type 1: RMS Values

Q1: Peak current = 5 A. Find RMS.

$$I_{rms} = \frac{5}{\sqrt{2}} = 3.54A$$

Type 2: Reactance

Q2: L = 0.1 H, f = 50 Hz. Find XL.

$$X_L = 2\pi fL = 2\pi \cdot 50 \cdot 0.1$$

$$= 31.4\Omega$$

★ Type 3: Impedance

Q3: $R = 20\Omega$, $X_L = 40\Omega$, $XC = 10\Omega$. Find Z .

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{20^2 + 30^2} = \sqrt{400 + 900} = \sqrt{1300} \\ Z &= 36.05\Omega \end{aligned}$$

★ Type 4: Resonance

Q4: $L = 2 \text{ mH}$, $C = 5 \mu\text{F}$. Find resonance frequency.

$$\begin{aligned} f_r &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{2 \times 10^{-3} \cdot 5 \times 10^{-6}}} \\ &= 1591 \text{ Hz} \end{aligned}$$

★ Type 5: Power in AC

Q5: $V = 220 \text{ V}$, $I = 5 \text{ A}$, $\cos\phi = 0.8$.

$$P = VI \cos\phi = 220 \times 5 \times 0.8 = 880W$$

★ 4. PAST YEARS' BOARD QUESTIONS (SOLVED)

(Based on CBSE trends 2014–2024)

✓ Q1

State RMS value.

(1 mark — very common)

✓ Q2

Define reactance and impedance.

(2 marks)

✓ Q3

Draw phasor diagram of R-L series circuit.
(3 marks)

✓ Q4

Explain resonance in LCR circuit.
(3 marks)

✓ Q5

Derive expression for impedance of LCR circuit.
(5 marks)

✓ Q6

A numerical on X_L or X_C .
(Almost every year)

✓ Q7

AC power expression derivation.
(4 marks)

★ 5. QUICK REVISION NOTES (1–2 PAGES)

rainbow AC Basics

- AC varies sinusoidally.
 - RMS = peak/ $\sqrt{2}$
 - $\omega = 2\pi f$
-

rainbow Circuit Elements

Element	Phase Relation	Reactance
R	I & V in phase	R
L	I lags	$X_L = \omega L$
C	I leads	$X_C = 1/\omega C$

rainbow LCR Circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance

- Occurs when $X_L = X_C$
 - Z minimum, I maximum
 - Used in tuning radios
-

Power

- Instantaneous power fluctuates
 - Average power = $VI \cos \phi$
 - Power factor important for efficiency
-

6. PREDICTED / LIKELY QUESTIONS (2025 Boards)

Short Answer

- Define RMS value
- What is reactance?
- Difference between AC & DC
- Write formula for impedance
- Explain resonance

Long Answer

- Derive RMS value
- Derive impedance of LCR circuit
- Derive power in AC circuit
- Explain phasor diagrams

Numerical

- X_L , X_C
 - Impedance
 - Power factor
 - RL/RC/LCR circuit current
-

7. EXAM TIPS & TRICKS

✓ Tip 1

Use **ELI-ICE** for phase:

- Voltage leads in **L**
- Current leads in **C**

✓ Tip 2

Always convert $\text{mH} \rightarrow \text{H}$, $\mu\text{F} \rightarrow \text{F}$.

✓ Tip 3

In resonance problems:

- $Z = R$
- $I = \text{maximum}$

✓ Tip 4

Phasor diagrams = easy scoring.

Draw clean arrows.

✓ Tip 5

Before solving AC problems, identify:

- R?
- L?
- C?
- Series or parallel?

★ 8. VISUAL & KID-FRIENDLY MEMORY TOOLS

🎨 Visual: AC Wave

Positive - Zero - Negative - Zero - Repeat

🎨 Visual: L vs C Phase

L: heavy coil \rightarrow current slow

C: storage tank \rightarrow current fast

🎨 Visual: Resonance

L & C cancel each other → only R left → max current

Visual: Impedance Triangle

$$\begin{array}{ccc} & Z & \\ / & \backslash & \\ R & & (XL - XC) \end{array}$$