

CURRENT ELECTRICITY – FULL STUDY GUIDE (CLASS 12)

 *Easy → Visual → Exam-Focused → Beginner-Friendly*

1. THEORY IN SIMPLE WORDS (WITH VISUALS)

1.1 What is Electric Current?

Electric current = **flow of electric charges (electrons)** in a conductor.

Symbol:

$$I = \frac{Q}{t}$$

Analogy:

Think of electrons as **water** flowing in a pipe.

Visual:

Battery → → → Electrons → → → Bulb

1.2 Electric Current Direction

- Electrons flow **from – to +**
- Conventional current is taken **from + to –**

Visual:

+ → → → conventional current
← ← ← electrons

1.3 Drift Velocity

Average velocity with which electrons move in a conductor under electric field.

$$v_d = \frac{I}{nAe}$$

Where:

n = number density of electrons

A = area of cross section

e = charge of electron

Analogy:

Like students slowly drifting toward the exit after school.

1.4 Mobility (μ)

How easily electrons move.

$$\mu = \frac{v_d}{E}$$

1.5 Ohm's Law

$$V = IR$$

Meaning:

Voltage \propto Current (if temperature constant)

Visual:

More R = harder for charges to pass (thin pipe)

Less R = easier (thick pipe)

1.6 Resistance (R)

Opposition to the flow of charges.

$$R = \rho \frac{L}{A}$$

Where ρ = resistivity (property of material)

1.7 Resistivity (ρ)

- Depend on material only
 - Unit: Ωm
 - Metals \rightarrow low ρ
 - Insulators \rightarrow high ρ
-

1.8 Temperature Dependence

For metals:

Temperature $\uparrow \rightarrow$ resistance \uparrow

For semiconductors:

Temperature $\uparrow \rightarrow$ resistance \downarrow

Visual:

Heat = vibrations = electrons hitting atoms more = more resistance

1.9 Electrical Power

$$P = VI = I^2R = \frac{V^2}{R}$$

1.10 EMF & Potential Difference

EMF (E):

Work done per unit charge in maintaining current in circuit.

Potential Difference (V):

Energy used by charge between two points.

Difference:

- EMF \rightarrow source/battery
 - PD \rightarrow used by components
-

1.11 Internal Resistance

Resistance inside battery.

Visual:

(Battery) [r] ---- external circuit

Terminal voltage:

$$V = E - Ir$$

1.12 Series & Parallel Combination of Resistors

Series:

$$R_s = R_1 + R_2 + \dots$$

Parallel:

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

Visual:

Series: one path

Parallel: multiple paths

2. KEY CONCEPTS & FORMULAS TABLE

Concept	Formula	Trick
Current	$I = Q/t$	"Flow per sec"
Drift velocity	$v_d = I/(nAe)$	I on top
Mobility	$\mu = v/E$	"Velocity per field"
Ohm	$V = IR$	TRIANGLE: V on top
Resistance	$R = \rho L/A$	Long ↑ = R↑, Thick ↑ = R↓
Resistivity	$\rho = RA/L$	Material only
Power	$P = VI, I^2R, V^2/R$	V = IR transform
EMF relation	$V = E - Ir$	Loss in battery
Series	$R = R_1 + R_2$	add directly
Parallel	$1/R = 1/R_1 + 1/R_2$	"Cross-multiply shortcut"
Conductance	$G = 1/R$	reciprocal

Mnemonics

For Ohm's Law Triangle

V
I R

For Resistance: "L over A"

- Longer → harder
- Wider → easier

For series/parallel:

RES-SER, CAP-PAR

(Resistors add in Series)

3. SOLVED NUMERICAL PROBLEMS

★ Type 1: Ohm's Law

Example:

A 10Ω resistor is connected to 5V. Find current.

$$I = V/R = 5/10 = 0.5A$$

★ Type 2: Resistance using ρ

Example:

A wire of length 2m, area $1 \times 10^{-6}m^2$, resistivity $2 \times 10^{-6}\Omega m$. Find resistance.

$$\begin{aligned} R &= \rho \frac{L}{A} \\ &= 2 \times 10^{-6} \cdot \frac{2}{1 \times 10^{-6}} \\ &= 4\Omega \end{aligned}$$

★ Type 3: Power

Example:

Current = 3A, R = 4Ω. Find power.

$$P = I^2 R = 9 \cdot 4 = 36W$$

★ Type 4: EMF & internal resistance**Example:**

E = 12V, r = 1Ω, current = 2A. Find terminal voltage.

$$V = E - Ir = 12 - 2 = 10V$$

4. PAST YEAR BOARD QUESTIONS (SOLVED)

(Based on common CBSE trends)

✓ Q1 (2023)

State Ohm's law. Define resistance.

Ans: $V \propto I$ if temperature constant; $V = IR$.
Resistance = opposition to flow of current.

✓ Q2 (2022)

Explain drift velocity and relation with current.

Ans:

$$I = nAve_d$$

✓ Q3 (2021)

Derive equivalent resistance in series.

(Write voltages add, current same → sum of resistances.)

✓ Q4 (2020 – Numerical)

A 5Ω and 10Ω resistors connected in parallel. Find equivalent R.

$$\frac{1}{R} = \frac{1}{5} + \frac{1}{10}$$

$$R = 3.33\Omega$$

✓ Q5 (2019)

Define EMF and terminal voltage.

(Write definitions + formula $V = E - Ir$.)

5. QUICK REVISION NOTES (1–2 PAGE STYLE)

☀ Current

- Flow of charges
- $I = Q/t$
- Direction: $+$ \rightarrow $-$ (conventional)

☀ Drift Velocity

- Slow movement
- $I = nAve_d$

☀ Resistance

- $R = \rho L/A$
- ρ depends on material

☀ Temperature Effect

- Metals: $R \uparrow$ with $T \uparrow$
- Semiconductors: $R \downarrow$ with $T \uparrow$

☀ Ohm's Law

- $V = IR$
- Straight line V – I graph

☀ Power

- $P = I^2R$ (useful in numericals!)

☀ EMF & Internal Resistance

- $V = E - Ir$
- Terminal voltage $<$ EMF unless $I = 0$

☀ Series/Parallel

- Series → R increases
 - Parallel → R decreases
-

6. PREDICTED / LIKELY QUESTIONS (2025 BOARD TREND)

Short Questions

- Define drift velocity
- Define mobility
- Write relation between current & drift velocity
- State Ohm's law
- What is resistivity?

Long Questions

- Derive $R = \rho L/A$
- Derive series/parallel formulas
- Discuss temperature dependence of resistance

Important Numericals

- Ohm's law (easy scoring)
 - Power & energy
 - Using ρ to calculate R
 - EMF & internal resistance
-

7. EXAM TIPS & TRICKS

✔ Tip 1:

Always check units (most marks lost here!)

✔ Tip 2:

Convert $\text{mm}^2 \rightarrow \text{m}^2$ (area unit mistakes common in ρ problems).

✔ Tip 3:

For parallel resistors (two only), use shortcut:

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

✔ Tip 4:

Draw V-I graph when asked: straight line through origin = Ohmic conductor.

✓ Tip 5:

In EMF problems, first find current, then terminal voltage.

8. VISUAL & KID-FRIENDLY MEMORY TOOLS

Visual 1: Resistance

Thin wire → high R

Thick wire → low R

Visual 2: Current Flow

River flow → electrons flowing

Visual 3: Parallel vs Series

Series: one road

Parallel: many roads

Visual 4: Power

"More current = more heat"

$$\img alt="flame icon" data-bbox="82 578 100 592"/> $P = I^2 R$$$